

22326

12425

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following :

10

- (a) Give the application of power transistor (any four).
- (b) Draw V-I characteristics for : TRIAC.
- (c) Give the applications of SMPS (any four).
- (d) State any four methods of SCR triggering.
- (e) Draw symbols of IGBT and GTO.
- (f) Define :
 - (i) Firing Angle
 - (ii) Conduction Angle
- (g) State the need of UPS.



2. Attempt any THREE of the following : 12

- (a) Describe with neat sketch the constructional details of IGBT.
- (b) Explain the operation of single phase fully controlled midpoint configuration rectifier with RL load.
- (c) Compare SCR & TRIAC (any four).
- (d) How SCR commutates in class A method ? Explain with diagram.

3. Attempt any THREE of the following : 12

- (a) Draw and explain two transistor analogy of SCR.
- (b) Draw circuit diagram of UJT triggering of SCR and draw waveform to show firing angle control.
- (c) Draw circuit diagram of battery charger circuit using SCR. Explain its working.
- (d) Explain the operation of 1- ϕ fully controlled bridge converter with “R” load.

4. Attempt any THREE of the following : 12

- (a) Explain auxiliary commutation with a neat diagram. Also draw its waveform.
- (b) Explain the operation of UPS with a neat block diagram.
- (c) Explain the operation of crowbar circuit for overvoltage protection with neat diagram.
- (d) A single phase fully controlled rectifier supplied with voltage $V = 200 \sin 314 t$, $\alpha = 30^\circ$ and load resistance 60Ω . Find :
 - (i) Average output DC voltage and
 - (ii) Load current
- (e) Describe emergency lighting system with neat diagram.

5. Attempt any TWO of the following :**12**

- (a) Draw and explain V-I characteristics of SCR and define the following terms :
 - (i) Forward break over voltage
 - (ii) Latching current
 - (iii) Holding current
- (b) Explain pulse transformer and opto coupler based triggering of SCR.
- (c) Draw and explain the working of $I-\phi$ half wave controlled rectifier with RL load. Explain the effect of freewheeling diode.

6. Attempt any TWO of the following :**12**

- (a) Draw the circuit diagram of DC static circuit breaker and give its operation.
 - (b) State classification of phase controlled rectifier. Also differentiate between controlled and uncontrolled rectifiers (4 points).
 - (c) Draw symbol and V-I characteristics of :
 - (i) LASCR
 - (ii) SCS
 - (iii) DIAC
-

