

22331

12425

03 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

-
- Instructions* – (1) All Questions are *Compulsory*.
(2) Answer each next main Question on a new page.
(3) Illustrate your answer with neat sketches wherever necessary.
(4) Figures to the right indicate full marks.
(5) Assume suitable data, if necessary.
(6) Use of Non-programmable Electronic Pocket Calculator is permissible.
(7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following: 10
- a) State functions of:
 - i) Electron gun
 - ii) Phosphor screen.
 - b) Classify the instruments.
 - c) List specifications of digital voltmeter. (Any two)
 - d) List the applications of PMMC meter. (Any two)
 - e) State the function of delay line in CRO.
 - f) List different types of CRO. List any two applications of CRO.
 - g) Define resolution of DVM.

P.T.O.

- 2. Attempt any THREE of the following:** **12**
- a) Explain the working of PMMC instrument.
 - b) Explain the operation of a digital frequency meter with a neat labelled diagram.
 - c) Explain how time period and frequency can be measured using CRO.
 - d) Explain the procedure to measure unknown inductance using Hay's bridge with neat circuit diagram.
- 3. Attempt any THREE of the following:** **12**
- a) Define calibration and state its need.
 - b) Draw the circuit diagram of conversion of PMMC to multirange current meter. Derive equation for shunt resistance.
 - c) Explain spectrum analyzer with neat block diagram.
 - d) Explain the significance of Lissajous pattern with appropriate example.
- 4. Attempt any THREE of the following:** **12**
- a) Draw and explain LCR meter with neat block diagram.
 - b) Draw the basic block diagram of signal generator and explain the function of each block.
 - c) Compare analog instruments and digital instruments. (Four points)
 - d) Explain series type Ohmmeter with neat diagram.
 - e) Draw neat and labelled diagram of cathode ray tube (CRT).
- 5. Attempt any TWO of the following:** **12**
- a) Explain the working of Wheatstone's bridge with neat circuit diagram and state which parameter can be measured using Wheatstone's bridge.
 - b) Write two specifications of analog multimeter. Also convert PMMC movement into DC voltmeter of the range 0 to 100 MV.
 - c) Draw and explain block diagram of DSO.

6. Attempt any TWO of the following:**12**

- a) Draw and explain the operation of successive approximation type DVM. (Assume SAR register as a 3 bit)
 - b) Describe the classification of the characteristics of instruments and define following characteristics:
 - i) Accuracy
 - ii) Error
 - iii) Fidelity
 - iv) Lag.
 - c) Draw neat and labelled diagram of full wave rectifier and explain the working of it.
-