

22427

12425

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.

Marks

1. Attempt any FIVE of the following :

5 × 2 = 10

- (a) Draw V-I characteristics of IGBT and label the different regions.
- (b) Draw the symbols of (i) GTO (ii) SUS.
- (c) State difference between forced commutation and natural commutation. (Any two points)
- (d) State any two applications of controlled rectifiers.
- (e) List two applications of choppers.
- (f) Define Inverter. Classify it.
- (g) List any two advantages of UPS.

2. Attempt any THREE of the following :

3 × 4 = 12

- (a) Draw V-I characteristics of SCR and define holding current and latching current.
- (b) Draw block diagram of SMPS and describe its working.
- (c) Explain working of step-up chopper with neat diagram.
- (d) Describe the operation of single phase half wave controlled rectifier with R-L load.



3. Attempt any THREE of the following : 3 × 4 = 12

- (a) Draw the circuit of class A commutation for SCR and describe its operation.
- (b) Describe the effect of free wheeling diode in controlled rectifiers.
- (c) Compare step-up and step-down chopper with respect to following parameters :
 - (i) Range of output voltage
 - (ii) Expression of output voltage
 - (iii) Quadrant of operation
 - (iv) Applications
- (d) Draw the neat circuit diagram of emergency light system and write its working.

4. Attempt any THREE of the following : 3 × 4 = 12

- (a) State turn ON methods of SCR. Explain dv/dt triggering.
- (b) A single phase full wave controlled rectifier is supplied with a voltage $V = 230 \sin(314 t)$. Find average DC output voltage and current if firing angle is 45° and load resistance is 100Ω .
- (c) With a neat diagram, explain the operation of step-down chopper using MOSFET.
- (d) Draw with neat circuit diagram lamp dimmer circuit using DIAC-TRIAC and explain its working.
- (e) Draw the circuit of R-triggering of SCR and explain its working.

5. Attempt any TWO of the following : 2 × 6 = 12

- (a) Draw labelled constructional diagram for GTO and describe its working with V-I characteristics.
- (b) Draw and explain SCR triggering using UJT with the help of pulse transformer. List its advantages.
- (c) Explain the operation of 3-phase half wave controlled rectifier with R-load with circuit diagram. Draw its input and output voltage waveforms.

6. Attempt any TWO of the following : 2 × 6 = 12

- (a) Describe the working of Series Inverter with neat diagram and state its two applications.
 - (b) Describe the working principle of power MOSFET using constructional diagram. Draw the V-I characteristics of Power MOSFET.
 - (c) Suggest a suitable power device having 1st and 3rd quadrant symmetrical characteristics and describe its operation with modes.
-