22212

12425 3 Hours / 70 Marks

Seat No.

Instructions : (1) All Questions are *compulsory*.

- (2) Answer each next main Question on a new page.
- (3) Illustrate your answers with neat sketches wherever necessary.
- (4) Figures to the right indicate full marks.
- (5) Assume suitable data, if necessary.
- (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
- (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

1. Attempt any FIVE :

- (a) Define "Electric Current" and express it mathematically.
- (b) State "Ohm's law" and express it mathematically.
- (c) Define "Breakdown voltage" and state its unit.
- (d) Define "MMF" and state its unit.
- (e) Define "Reluctance" and state its unit.
- (f) State "Fleming's Right Hand rule".
- (g) State "Lenz's rule".

2. Attempt any THREE :

- (a) With neat diagram, explain magnetic effect of electric current flowing through –
 (i) Straight conductor (ii) Coil.
- (b) With a neat circuit diagram, explain the terms :
 - (i) Node (ii) Branch (iii) Loop (iv) Mesh.



Marks

10

[2 of 4]

- (c) Derive an equation for energy stored in a capacitor.
- (d) With the help of neat circuit diagram, explain the concept of :(i) Self-induced emf. (ii) Mutually induced emf.

3. Attempt any THREE :

- (a) With neat diagram and suitable example, explain chemical effect of electric current.
- (b) Calculate the resistance of a 100 m length of wire having a uniform crosssectional area of 0.02 mm² and having resistivity of 40 $\mu\Omega$ cm. If the wire is drawn out to four times its original length, calculate its new resistance.
- (c) Distinguish between :
 - (i) Active circuit and Passive circuit.
 - (ii) Unilateral circuit and Bilateral circuit.
- (d) Derive an equation for capacitance of parallel plate capacitor.

4. Attempt any THREE :

- (a) A bulb rated 230 V, 60 W is connected in series with another bulb rated 230 V, 100 W. If this combination is connected across 230 V supply, calculate energy consumed by each bulb in 2 hrs.
- (b) Calculate the terminal voltage of a battery source having emf of 12 V, internal resistance of 1 Ω and load resistance of 9 Ω . Also calculate the load current.
- (c) Applying Kirchhoff's laws, find the potential difference between points X and Y in the network shown in Fig.1 :



Fig. 1

22212

12

(d) A 100 μ F capacitor is being charged through 10 k Ω resistor from 100 V dc supply.

Determine :

- (i) Charging time constant
- (ii) Initial value of charging current
- (iii) Voltage and current of capacitor after 5 millisecond from the start of charging.
- (e) Two capacitors 100 μ F and 50 μ F are connected in parallel. This parallel combination is then connected in series with a 200 μ F capacitor. Finally this series parallel combination is connected across 100 V dc supply.

Calculate :

- (i) Voltage across each capacitor
- (ii) Charge on each capacitor
- (iii) Energy stored in each capacitor.

5. Attempt any TWO :

- (a) State any four similarities and any two differences between electric circuit and magnetic circuit.
- (b) An iron ring has a circular cross-section of 300 mm² and a mean diameter of the ring is 200 mm. It is uniformly wound with 800 turns of copper wire. Relative permeability is 500.

Calculate :

- (i) Magnetic field strength produced in the core by a current of 3 A.
- (ii) Magnetic flux density produced by this current.
- (iii) The current required to produce a flux density of 0.8 Wb/m^2 .
- (c) Two coils, A of 12000 turns and B of 15000 turns, lie in parallel planes such that 60% of the flux produced by coil A links with coil B. A current of 5 A in coil A produces a flux of 0.05 mWb, while the same current in coil B produces a flux of 0.075 mWb.

Find :

- (i) Self-inductance of each coil
- (ii) Mutual inductance
- (iii) Coefficient of coupling.

[4 of 4]

6. Attempt any TWO :

- (a) Determine the mmf, flux, reluctance and flux density in the steel ring of 30 cm mean diameter and a circular cross-section of 2 cm diameter. It has an airgap of 1 mm length. It is wound with a coil of 600 turns carrying a current of 2.5 A. Neglect magnetic leakage. The iron path takes 40% of total mmf.
- (b) Two coils, A and B, have self-inductances of 120 μ H and 300 μ H, respectively. A current of 1 A through coil A produces flux-linkages of 100 μ Wb-turns in coil B.

Calculate :

- (i) Mutual inductance between the coils.
- (ii) The coupling coefficient
- (iii) The average emf induced in coil B if a current of 1 A in coil A is reversed at a uniform rate in 0.1 sec.
- (c) A flux of 0.5 mWb is produced in a coil of 900 turns wound on a ring by a current of 5 A. Another coil of 600 turns is wound uniformly over the first coil such that 80% of the flux produced by any one coil links with the other coil.

Calculate :

- (i) Self-inductance of each coil.
- (ii) Mutual inductance.
- (iii) Coefficient of coupling.
- (iv) Energy stored in first coil when it carries a current of 5 A.