

22216

12425

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--


- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following :

10

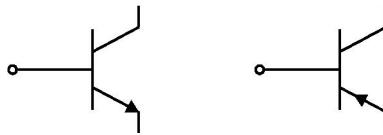- (a) State knee voltage value of Si and Ge Diode.
- (b) State the different types of filters used in Rectifiers.
- (c) Identify the following symbol of the components :



- (d) Define following terms w.r.t FET :
 - (i) Transconductance (I_m)
 - (ii) Amplification factor (μ)
- (e) List types of JFET and draw their symbols.
- (f) State the need of DC Regulated Power Supply.
- (g) Define Line Regulation and Load Regulation.



2. Attempt any THREE of the following :**12**

- (a) Define energy band and state the effect of temperature on it for a semiconductor with an example.
- (b) Sketch and explain the circuit diagram of Bridge Rectifier with input and output waveforms.
- (c) Explain the need of stabilization of Q point in case of transistor.
- (d) Sketch neat block diagram of a regulated power supply and explain the function of each block.

3. Attempt any THREE of the following :**12**


- (a) Compare P-N junction diode and Photodiode with the following parameters :
 - (i) Circuit Symbol
 - (ii) Material used
 - (iii) Biasing
 - (iv) Application
- (b) Define the following terms :
 - (i) Transformer Utilization factor
 - (ii) Ripple factor
 - (iii) Peak inverse voltage
 - (iv) Efficiency
- (c) Sketch and explain self-bias in transistor.
- (d) A 2N5668 JFET has $V_{GS(off)} = -4$ Volt and If $I_{DSS} = 5$ mA, what are the Gate voltage and drain current at half of cut-off point ?

4. Attempt any THREE of the following :**12**

- (a) Explain the working of Zener Voltage regulator with neat circuit diagram.
- (b) Compare Inductor filter and capacitor filter with the following parameters :
 - (i) Circuit diagram
 - (ii) Waveforms
- (c) Distinguish in between BJT and FET any four points.
- (d) Describe the principle of working D-MOSFET with neat circuit diagram.
- (e) Compare CB, CE and CC configuration.

5. Attempt any TWO of the following :**12**

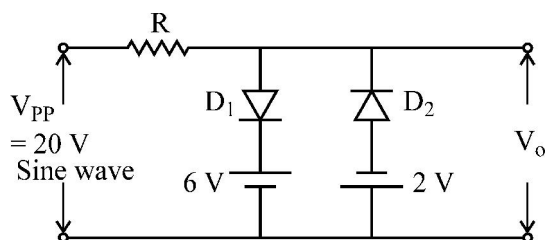- (a) Sketch the constructional diagram of LED and state the applications of LED.
- (b) Identify the following circuit and draw input and output waveforms :



- (c) Define α and β of BJT and derive the relation between α and β .

6. Attempt any TWO of the following :**12**

- (a) What is the operating point Q of transistor ? Draw DC load line on Output characteristics of BJT, and show different operating points on DC load line.
- (b) Explain Drain characteristics of JFET with Ohmic region, saturation region, cut-off region, breakdown region.
- (c) Draw the circuit diagram of transistorized series voltage regulator and explain its working.

