

22225

12425

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following :

10

- (a) Draw symbol of Inductor and Capacitor. State unit of both.
- (b) Draw symbol of JFET. State why it is called unipolar device.
- (c) State seebeck and Peltier effect.
- (d) Define Transducer. Name two passive transducers.
- (e) Write the classification of Electronic components.
- (f) Draw the V-I characteristic of Zener diode.
- (g) Define (i) Current gain (ii) Voltage gain for CE amplifier.

2. Attempt any THREE of the following :

12

- (a) Draw a neat diagram of Half-Wave Rectifier. Also draw input & output wave-form.
- (b) Describe working of NPN transistor along with constructional diagram.
- (c) Explain N-Channel JFET with suitable diagram.
- (d) Sketch block diagram of Regulated power supply & explain it's working.



3. Attempt any THREE of the following :**12**


- (a) Compare Active Transducer & Passive Transducer with example.
- (b) Draw and explain the circuit diagram of the Two stage RC coupled CE amplifier with waveform.
- (c) Write the colour codes of following resistor :
 - (i) 560 k, $\pm 2\%$ (ii) 23.4 k, $\pm 10\%$
- (d) Define α & β . Derive the relation between α & β .

4. Attempt any THREE of the following :**12**

- (a) Explain the working of Thermocouple with suitable diagram.
- (b) Sketch input & output V-I characteristic of CB & label the various regions.
- (c) Draw the neat labelled constructional diagram of LED & describe its working.
- (d) Give symbol, construction and working of P-channel JFET.

5. Attempt any TWO of the following :**12**

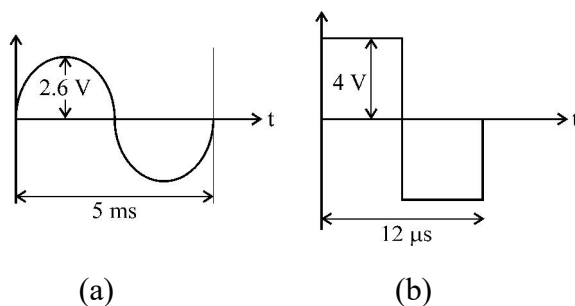- (a) (i) Differentiate between CE, CB, CC w.r.t.
 - 1. Current gain
 - 2. Voltage gain
 - 3. Input Resistance
 - 4. Output Resistance
- (ii) Define operating point of the Transistor.
- (b) Calculate peak to peak amplitude, frequency & wavelengths of waveform shown in fig. (a) & (b).



- (c) (i) Draw and explain the working of Bridge Rectifier with it's waveform.
(ii) Give Ripple factor and efficiency of Bridge Rectifier.

6. Attempt any TWO of the following :

12

- (a) (i) If α of transistor is 0.9, calculate β .
(ii) If β is 100, Calculate α
(iii) If $r_i = 40 \Omega$, $\Delta I_E = 5 \text{ mA}$

Calculate ΔV_{EB}

- (b) Draw the Drain characteristics of JFET.

Define :

- (i) Amplification factor
(ii) Transconductance
(iii) AC Drain Resistance
(iv) DC Drain Resistance
- (c) Explain Inductive proximity sensor with constructional diagram & working.
-

