

22346

23124

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following :

10

- (a) Draw symbol and construction of npn transistor.
- (b) Write the classification of power amplifier.
- (c) State Barkhausen criterion for sustained oscillations.
- (d) In an RC phase shift oscillator the value of resistor $R = 10 \text{ k}\Omega$ and capacitor $C = 3.25 \text{ nF}$. Calculate frequency of oscillation.
- (e) Write classification of wave shaping networks.
- (f) Define load regulation. Write its value for ideal voltage regulator.
- (g) Using IC 78XX/79XX, draw voltage regulator circuit to provide 12V dc output voltage.



2. Attempt any **THREE** of the following :


12

- Draw npn transistor in Common Base (CB) configuration. Name input, output voltages and currents with their directions. Write formula for current gain.
- Draw equivalent circuit and V-I characteristics of UJT.
- Draw circuit of common source FET amplifier. State function of each element.
- Draw drain characteristics of JFET and describe channel ohmic region and pinch-off region.

 3. Attempt any **THREE** of the following :

12

- Describe method to calculate current gain of transistor in CE configuration (β_{dc} , β_{ac}) with the help of output characteristics of transistor.
- Describe operating principle of E-MOSFET.
- Draw circuit of UJT relaxation oscillator. Draw waveforms at each terminal of UJT.
- Observe given integrator circuit. State whether it provides good integration or not. Give justification.



$$R = 10 \text{ k}\Omega \quad C = 0.01 \text{ }\mu\text{F}$$

Fig. 1

4. Attempt any THREE of the following :

12

- (a) Observe the given circuit. Write the state of LED when switch(s) is open and when switch(s) is closed. State the function of transistor in this circuit.


 


Fig. 2

 - (b) A JFET is to be used as an amplifier, in which operating region should be biased. Draw its biasing circuit and describe it.
- (c) Draw frequency response of single stage CE amplifier. Write the steps to calculate bandwidth of CE amplifier.
- (d) Suggest the multistage amplifier for audio signal amplification. Draw its circuit diagram.
- (e) For the given zener diode shunt regulator circuit. Calculate :
- The load voltage V_{RL}
 - Voltage drop across series resistance V_{RS}
 - Load current I_L
 - Zener current I_Z



$$R_S = 240 \, \Omega \quad V_Z = 12 \, \text{V}$$

$$V_S = 30 \, \text{V} \quad R_L = 500 \, \Omega$$

Fig. 3

5. Attempt any TWO of the following :


12

- Define thermal run-away of BJT. Draw voltage divider bias circuit and describe, how this bias circuit provides bias stability against temperature change.
- Draw and describe operation of Class-B push-pull power amplifier. Define cross-over distortion. Draw input & output voltage waveforms showing cross-over distortion.
- Define clamper. Draw and describe negative clamper circuit. Draw input and output waveforms for sine wave input.

 6. Attempt any TWO of the following :

12

- Draw block diagram of voltage series and voltage shunt feedback connection. State their effect on parameters of amplifier.
- Observe the given circuit. A square wave input of 100 Hz frequency is applied to it. Draw input waveform, waveform at point A and waveform at point B. Name the circuit.



$$C = 0.1 \mu\text{F}$$

$$R = 1 \text{ k}\Omega$$

Fig. 4

- Draw transistorised series voltage regulator with error amplifier. Describe how the output voltage is regulated if there is a drop in input voltage because of some reason. State the draw-back of linear regulator.