

22371

23124

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
  - (2) Illustrate your answers with neat sketches wherever necessary.
  - (3) Figures to the right indicate full marks.
  - (4) Assume suitable data, if necessary.
  - (5) Use of Non-programmable Electronic Pocket Calculator is permissible.

**Marks**

**1. Attempt any FIVE of the following :**

**10**

- (a) Draw V-I characteristics of Zener diode.
- (b) Draw symbols of NPN & PNP transistors.
- (c) State types of rectifiers.
- (d) Define unipolar and bipolar devices.
- (e) List different types of number system.
- (f) Convert following into 2's complement  $(1001)_2$ .
- (g) Draw pin diagram of IC 0808.

**2. Attempt any THREE of the following :**

**12**

- (a) Explain V-I characteristics of Zener diode with the help of circuit diagram.
- (b) Compare L and C filter on the basis of following parameters :
  - (i) Position of component in the circuit
  - (ii) Ripple formula
  - (iii) Circuit diagram
  - (iv) Advantage
- (c) Draw and explain full adder.
- (d) Draw symbol and truth table of NOR and NAND gate.



- 3. Attempt any THREE of the following : 12**
- (a) Draw and explain R-2R ladder type data converter.
  - (b) Draw a circuit diagram of +5V complete DC power supply formed by using IC 7805 and explain it.
  - (c) Draw a circuit of single stage RC coupled amplifier. Explain its working.
  - (d) Convert the following :
    - (i)  $(111101)_2 = (?)_{16}$
    - (ii)  $(25)_{16} = (?)_2$
  - (e) Draw and explain 8 : 1 multiplexer with truth table.
- 4. Attempt any THREE of the following : 12**
- (a) List different types of shift registers. Explain in detail Serial In Parallel Out (SIPO) register.
  - (b) Describe the working of centre tapped full wave rectifier with input and output waveforms.
  - (c) Derive the relationship between  $\alpha$  and  $\beta$ .
  - (d) 'NAND gate is called as Universal gate'. Justify this statement with any two examples.
  - (e) Draw the block diagram of dual slope ADC.
- 5. Attempt any TWO of the following : 12**
- (a) Explain T and D flip flop with diagram and truth table.
  - (b) Compare PN junction diode and Zener diode. (Any 6 points)
  - (c) Compare CB, CE and CC configurations of transistors. (Any 6 points)
- 6. Attempt any TWO of the following : 12**
- (a) Draw a complete block diagram of DC power supply and explain each block of power supply.
  - (b) Prove De Morgan's first and second theorem with statements.
  - (c) Describe Successive Approximation ADC.
-