

22629

23124

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Illustrate your answers with neat sketches wherever necessary.
 - (3) Figures to the right indicate full marks.
 - (4) Assume suitable data, if necessary.

Marks

1. Attempt any FIVE of the following :

10

- (a) State the need of electric drive.
- (b) Draw speed-torque characteristic of DC motors.
- (c) Compare Single phase SCR drives and Three phase SCR drives with any two performance parameters.
- (d) Draw circuit diagram of single phase semi-converter drive.
- (e) List different speed control methods used for three phase induction motors.
- (f) State the ratings & specifications of stepper motor drive.
- (g) State the selection criteria of microcontroller for electric drives.

2. Attempt any THREE of the following :

12

- (a) Explain the block diagram of basic elements of electric drives.
- (b) Compare half wave converter drive & full wave converter drive with four factors / points.
- (c) Draw and describe class B chopper drive.
- (d) With neat diagram explain stator voltage control method using thyristor circuit of three phase induction motor.



- 3. Attempt any THREE of the following :** **12**
- (a) State the selection criteria for the given type of electric drive.
 - (b) Draw the circuit of a three phase full converter drive. Draw the output waveform for voltage & current.
 - (c) Draw and describe class A chopper drive.
 - (d) Which type of drives are suitable for steel rolling mill ? Justify your answer.
- 4. Attempt any THREE of the following :** **12**
- (a) Explain the operation of basic chopper circuit using SCR.
 - (b) Which type of drives are used in sugar mill ? Explain with different stages.
 - (c) With neat diagram explain the operation of rotor resistance control using chopper for speed control method of AC motors.
 - (d) With neat diagram explain the operation of stepper motor drive employing microcontroller.
 - (e) Describe microprocessor based speed control method used for DC motor with neat diagram.
- 5. Attempt any TWO of the following :** **12**
- (a) Draw the circuit diagram of single phase dual converter using SCR and describe its operation with waveforms.
 - (b) Draw and describe four quadrant operation of chopper drive with waveforms.
 - (c) State any two advantages of microcontroller based drive. Draw labelled block diagram of Phase Lock Loop (PLL) control DC motor drive and state function of each block.
- 6. Attempt any TWO of the following :** **12**
- (a) Compare stator voltage control, constant V/F control and rotor resistance control. (Any 4 points)
 - (b) Explain with diagram/sketch the operation of chopper controlled D.C. drive in solar and battery powered vehicles.
 - (c) The single phase dual converter operated from 230-V, 50 Hz supply and the load resistance is $R = 10 \Omega$. The circulating inductance is $L_\gamma = 40 \text{ mH}$; delay angle is $\alpha_1 = 60^\circ$. Calculate the peak circulating current and the peak current, I_p of this converter circuit.
-