

Important Instructions to examiners:

- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given more Importance (Not applicable for subject English and Communication Skills).
- 4) While assessing figures, examiner may give credit for principal components indicated in the Figure. The figures drawn by candidate and model answer may vary. The examiner may give credit for any Equivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant Values may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case of some questions credit may be given by judgment on part of examiner of relevant answer based on candidate's understanding.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept.

Q1.

A) Answer any three:


12M

a) Explain the working of Luminance signal processing with circuit diagram.

Ans:-

Circuit diagram:-

02M

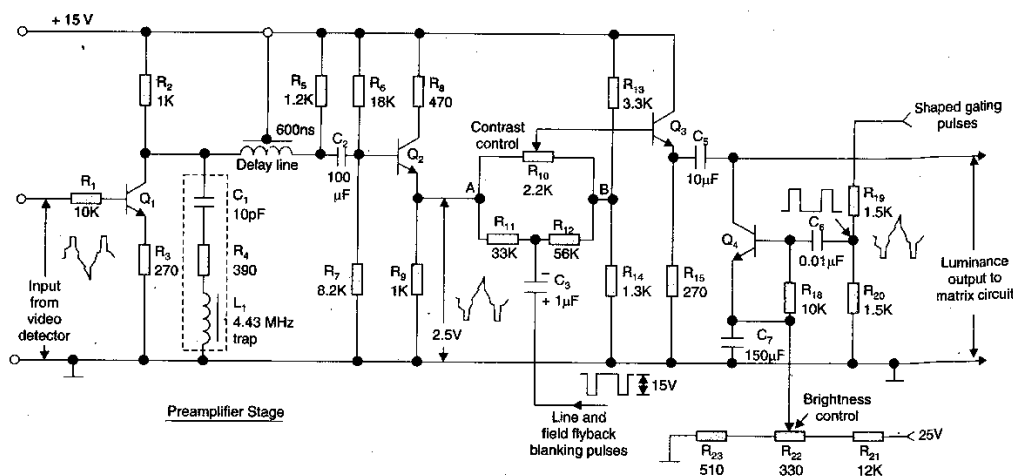

Working:

02M

- Transistor Q1 constitutes the preamplifier and it is designated to provide impedance match to the delay line on its output side and video detector on the input side.
- The amplified and inverted signal that becomes available at the collector of Q1 is fed via delay line at the base of Q2. The in between series trap formed by C1, R4 and L1 is to bypass Chroma signal.
- The contrast control elements R10, R11 and R12 form a part of a bridge circuit where potentials at point A and B are at the same level. The dc voltage at point A is nearly 3V and therefore values of R13 and R14 are so chosen that voltage at point B is also equal to 3 volts.
- The clamping voltages are applied directly to the emitter of Q4 which is connected to operate as an electronic switch. During picture content periods of the Y signal, the transistor is held in non-conducting

state by resistor R18 connected between base and emitter.


- During back porch intervals of the video signal, Q4 is momentarily forced into full conduction by the arrival of positive going line frequency rate pulses applied to its base via capacitor C6.
- The amplified video (luminance) signal obtained at the output of luminance channel is either passed on to a suitable stage in the Chroma IC or to the discrete R,G & B output stage.

b) Draw neat circuit diagram of sync separator and explain its working.

Ans:-

Circuit diagram:-

02M

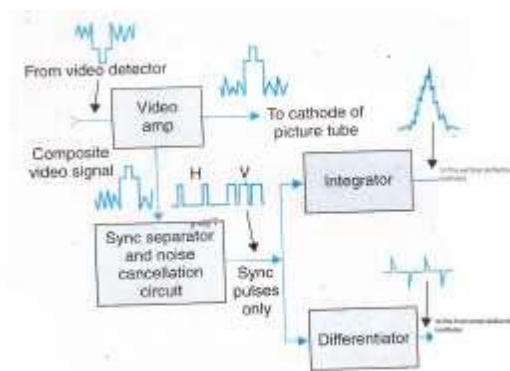

OR


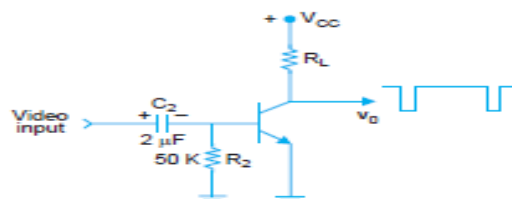


Fig. 16.2 (b). Basic sync separator circuit employing a transistor.

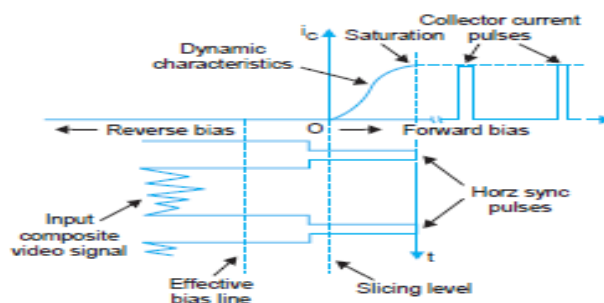

Explanation:-

02M

- The sync pulses include horizontal, vertical and equalizing pulses. These are separated from the video signal by the sync separator.
- The clipped line (horizontal) and field (vertical) pulses are processed by appropriate line-pulse and field-pulse circuitry. The sync output thus obtained is fed to the horizontal and vertical deflection oscillators to the time the scanning frequencies.
- As a result, picture information is in correct position on the raster.
- The sequence of the operation is illustrated in figure.
- The problem of taking off the sync pulses from the video waveform is a comparatively simple one, since the action consists of merely biasing the device used in the circuit, in such a way, that only the top portions of the video signal cause current flow in the device.


- This is readily achieved by self-biasing the tube or transistor use in the circuit.

c) Draw neat block diagram of microcontroller based TV system

Ans:-

Block Diagram:-

04M

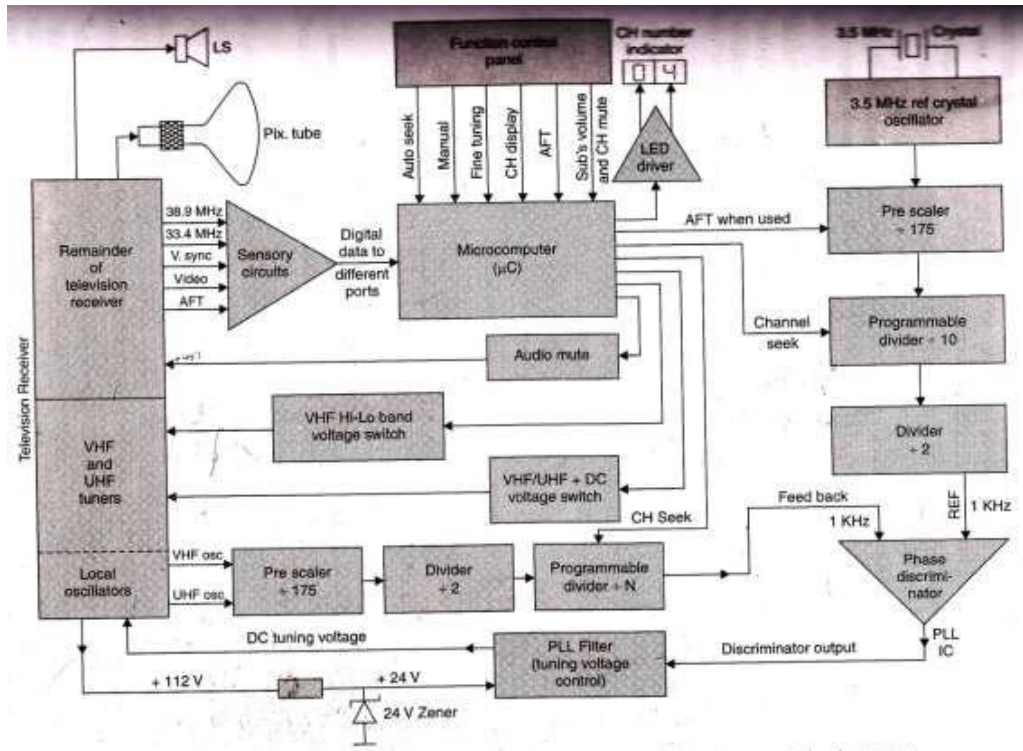

Explanation:-

02M

- The SAW filter uses two crystal, which have piezo-electric properties. When a varying electrical signal is applied across two surface of such a crystal, mechanical vibration are produced across the other opposite set of faces and vice versa. This characteristic has been made use of in the SAW filter.
- The transducing crystal is cut into segments, called fingers. All fingers are of the same length in the input transducer. Equal length of the fingers make it a broad band transducer

Q1

B) Attempt any one:


06M

a) Draw circuit diagram of ident signal amplifier and colour killer. Explain its working.

Ans:-

Diagram :-

03M

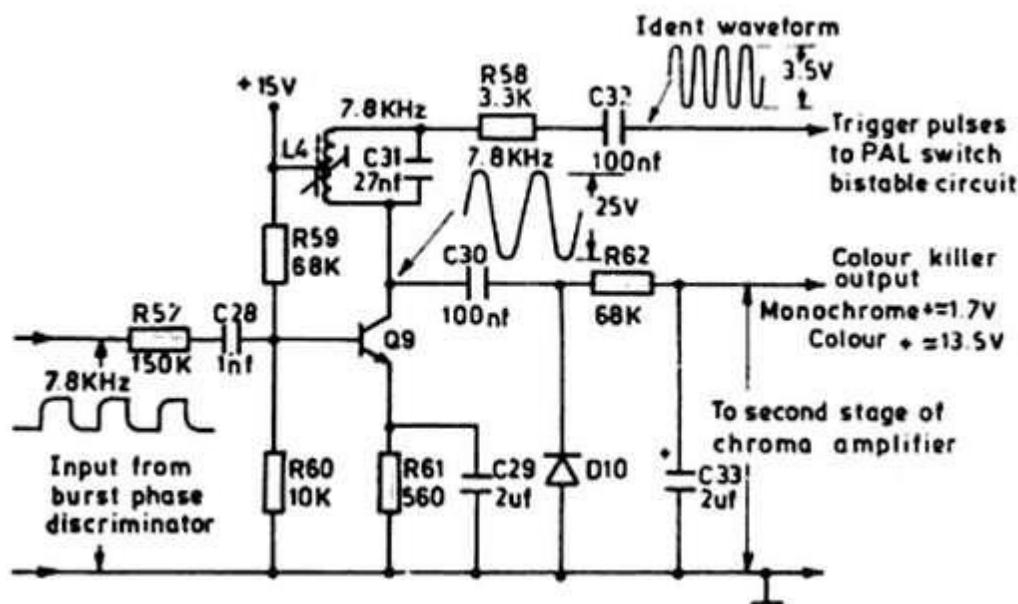

- any stray coloring signals are prevented from reaching RGB amplifier & hence, no colour noise appears on the black & white picture during monochrome receptions.

b) Explain auto stereoscopic method of 3 DTV. Write its one advantage. List different methods of auto stereoscopic.

Ans:-

Methods:-

½ M each

- Lenticular method
- Parallax method
- Holographic method

Advantage:-

01M


- No need to wear glasses to observe 3 D picture

Auto stereoscopic Method in 3DTV:-

(Explanation of

ii) Parallax Barrier:-

Diagram:-

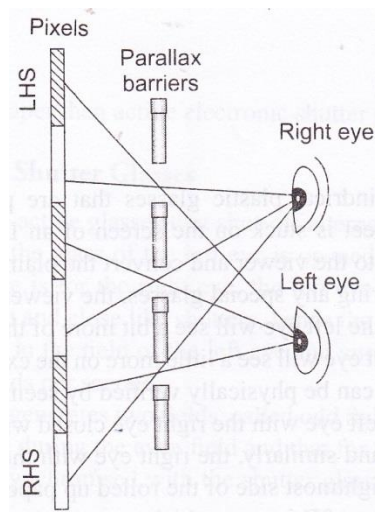

- The Parallax barrier is a fine grating of liquid crystal with slits in it. When placed over a screen, the slits corresponds to certain column of pixels on the TV's screen.
- When a small voltage is applied to the parallax barrier, the slitted grating allows two slightly different images to reach the left and the right eye, as shown in the fig. the brain processes these two images to produce 3D images.
- The parallax barrier can be switched on and off easily, allowing the TV to be used as a traditional 2D or A

- A laser beam from a suitable source, say an LED is split into two beams by a prism or a special mirror one beam goes to the object and is scattered from innumerable points of the object and reaches the film.
- The other beam from the splitter goes directly to the film without encountering the object. This is called "reference beam."
- As all the points of the object are not equidistant from the film, the scattered beam coming from non-equidistant point will have phase difference with respect to the reference beam from some point it would be in phase while from some other points out of phase.
- The phase, and weakening when they meet in an opposite phase. The interference pattern so obtained will produce the effect of depth. This is how holograms are prepared
- In case of TV, a 3D image will be registered on the surface of the target plate of the TV Camera by using holographic techniques.
- When this image is transmitted and reproduced on the display panel of the Tv receiver, it would be the hologram of the scene which this image is transmitted and reproduced on the display panel of the TV receiver, it would be the hologram of the scene which had been televised

Q2 Answer any four:

16M

a) Explain the generation of EHT using diode split technique


Ans:-

c) Describe the working of push pull SMPS with the help of block diagram

Ans:-

Block diagram:-

02M

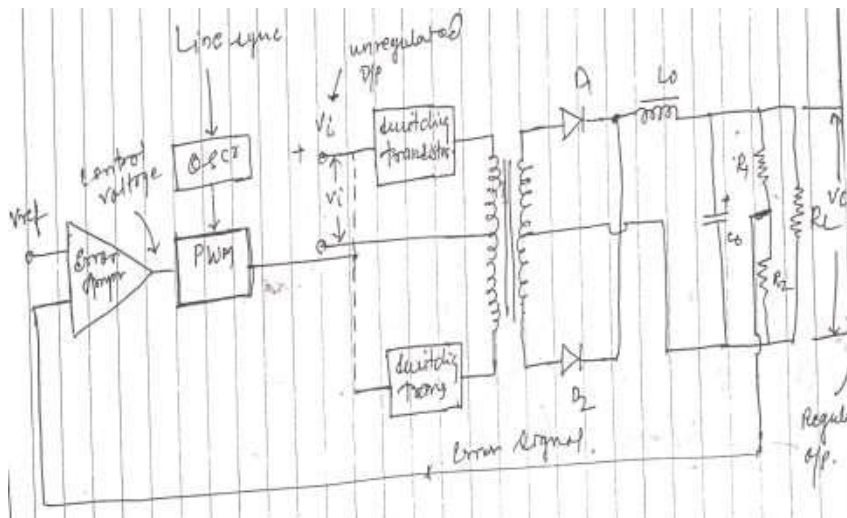



d) List advantages and disadvantages of remote control system.

Ans:-

Advantage:- (any two)

02M

- Audio muting option is available.
- TV can be programmed by remote control system.
- User can make their own set of selected channels.

Disadvantage :- (any two)

02M

- It requires line of site.
- Range of IR sensor is less compared to any other wireless communication components.
- Latest Tv do not have power on/OFF button on the Tv so if remote is faulty Tv cannot be stay off condition means it goes in standby mode which ultimately cause loss of power.

e) List characteristics and features of Plasma TV

Ans:-

Characteristic and Features of plasma TV: (any four)

A Schematic diagram of the remote control receiver is shown in fig. The pulse modulated infrared signals from the remote infrared transmitter are picked up by the remote infrared sensor D_1 . The picked up ac signal feeds into Q_1 , an FET amplifier, for some amplification. It is then coupled to the remote processor and pulse shaper via emitter follower Q_2 . The modulated signals are further amplified and then demodulated. The recovered pulse train then feeds into the pulse shaper which is designed to generate pulse patterns (ramps, high, low etc.). Each pattern is different and corresponds to the function button pressed on the remote control unit. The shaped individual pulse pattern is then dc coupled to the microcomputer. The microcontroller on receipt of different inputs produces appropriate output to perform the ordered functions.

Q.3 Attempt any four:

16M

(a) Draw circuit of forward SMPS and explain its working.


Ans:-



- The oscillator generates a rectangular pulse of constant duration & amplifier whose frequency is synchronized to the horizontal oscillator.
- The error amplifier controls the pulse width of pulse width modulation by applying controlled voltage. It compares reference voltage and error signal obtained from resistor voltage divider of R_1, R_2 to generate the control signal.
- When the transistor Q_1 is ON. Input voltage is applied to the primary winding of transformer T_1 or rising current in N_p produce polarity voltage. At the upper end N_s .
- Thus, diode D_1 conducts during ON period of transistor Q_1 to store energy in L_0 & C_0 & also feed load current. Diode D_2 stays reverse biased during this interval.
- As soon as transistor Q_1 turns 'OFF' the decreasing currents in N_p induces a voltage across N_s i.e. of opposite polarity.
- Diode D_1 is thus reverse biased & no transfer of energy to the load circuit takes place.
- However, the energy stored in L_0 and C_0 is transferred to the load circuit.
- Since the diode D_1 conducts & store energy when Q_1 is on, it is called as forward SMPS.

(b) Explain the role of microcontroller in TV receiver.

Ans:-

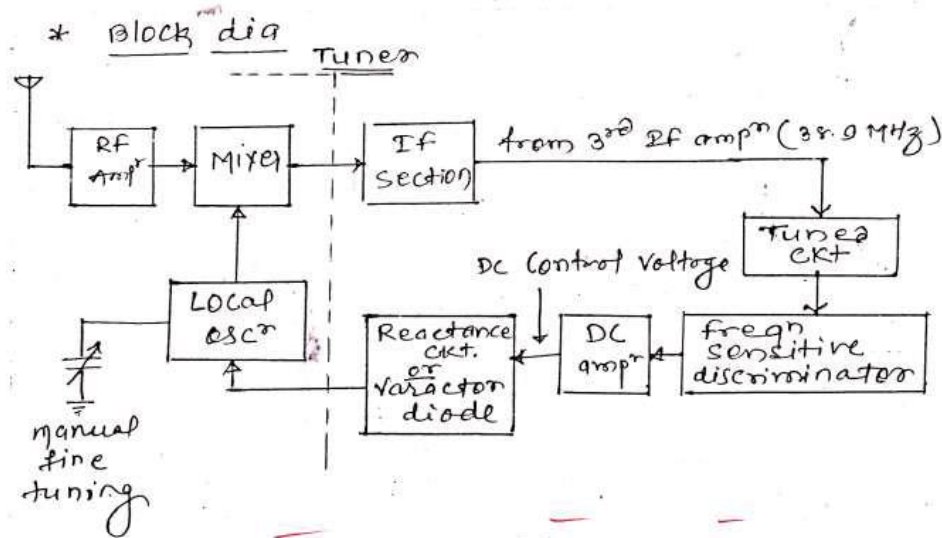

Explanation:-



	eye-strain	
Response Time	1–8 ms typical (according to manufacturer data), older units could be as slow as 35 ms	Sub-millisecond
Environmental Influences	Low temperatures can cause slow response, high temperatures can cause poor contrast	High altitude pressure difference may cause poor function or buzzing noises
Aging	Yes	Yes
Weight	Light	Heavy, however, less weight gain per size increase

Q.4

(A) Attempt any three:

12M

a) Explain the working of Trinitron picture tube with the help of well labeled diagram.

Ans:-

Diagram:-

02M



Explanation

02M

Need of reference oscillator in PAL- D decoder:

- The U and V Chroma signals are separately produced at the transmitting end by what is known as double-balanced suppressed-carrier modulator.
- Thus it is necessary to regenerate the subcarrier in the receiver to affect demodulation of colour difference signal.
- The reference oscillator circuit that generates a sinusoidal output at 4.43MHz is shown in figure above.
- The frequency is determined by the center-resonant frequency of the crystal (XL) which in this circuit is approximately 4.43MHz.